

ECE 215 Spring 2025

Objective 3.2:
Demodulation









UNITED STATES
AIR FORCE
ACADEMY

Objective 3.2

I can design a demodulator given a modulated signal for envelope and synchronous detection.

REMEMBER 3 FORMS OF AN AM SIGNAL

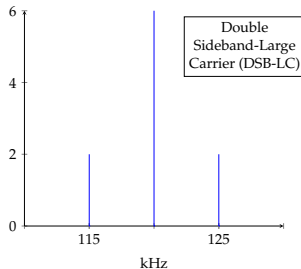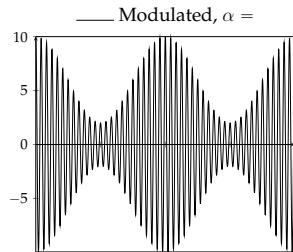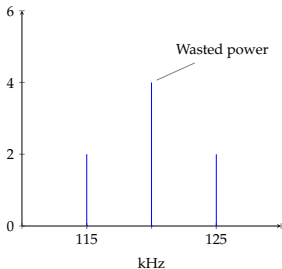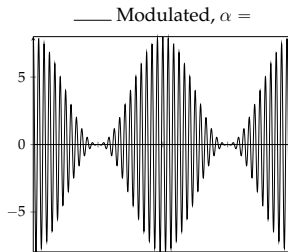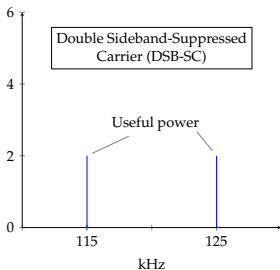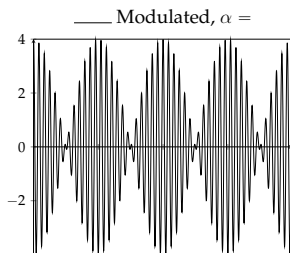

EFFICIENCY


- Recall the definition of efficiency:

$$\eta = \frac{P_{\text{useful}}}{P_{\text{useful}} + P_{\text{wasted}}} = \frac{P_{\text{upper sideband}} + P_{\text{lower sideband}}}{P_{\text{total}}}$$


- With modulation index of α , we have: $\eta = \frac{\alpha^2}{\alpha^2 + 2}$
- For bias = 0V : $\eta =$
- For fully modulated signal: $\eta =$
- As α decreases, efficiency decreases
- So why use 100% modulated or undermodulated signals?

TYPES OF DEMODULATORS

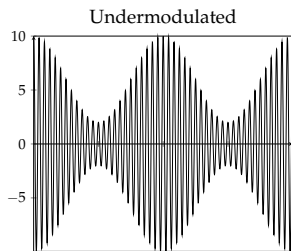- Demodulators “undo” the modulation we just did
- Synchronous detection (works for all AM signals)
 - Expensive, more complicated
- Envelope detector (works for 100% or undermodulated)
 - Cheap and easy to build




→ Demodulator →

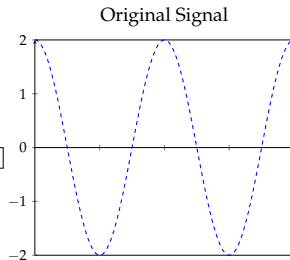

DEMODULATING OVERMODULATED SIGNALS

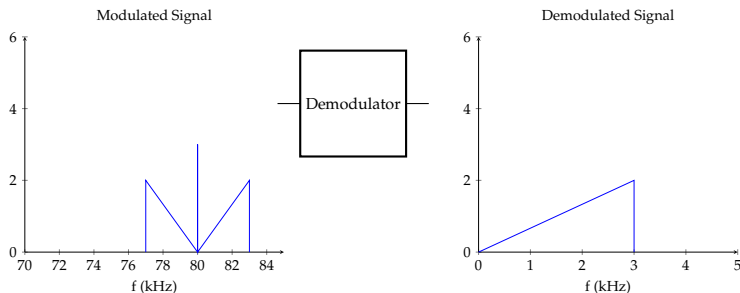
What is the modulation index of the modulated signal?



$$\alpha = \frac{A_m}{B} = \frac{2 * \left(\frac{A_c A_m}{2} \right)}{B A_c} =$$

SYNCHRONOUS DETECTOR

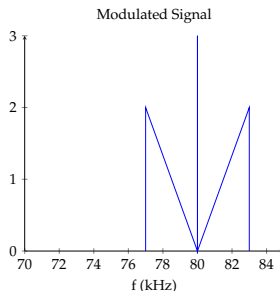
In the frequency domain, we have the following signal:



- What is the message signal?
- What is the carrier frequency?


SYNCHRONOUS DETECTOR

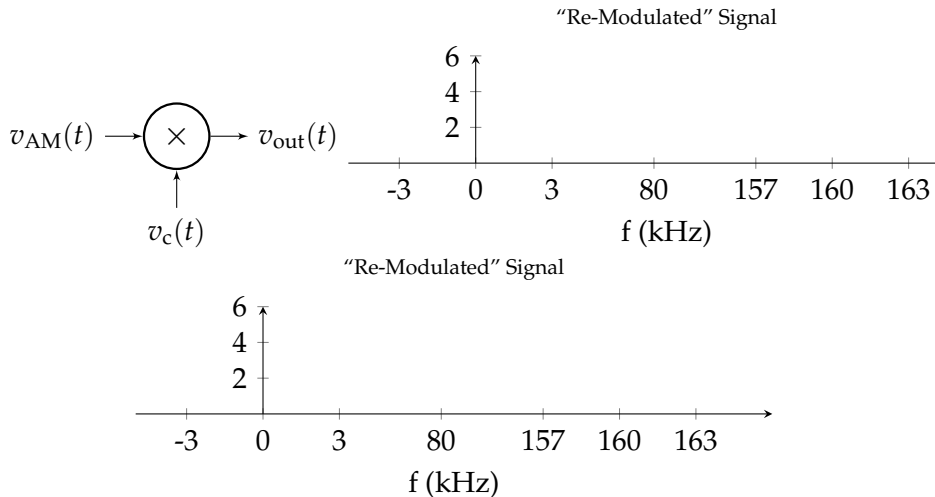Multiplying the received signal by the carrier frequency...




SYNCHRONOUS DETECTOR (CONT'D)

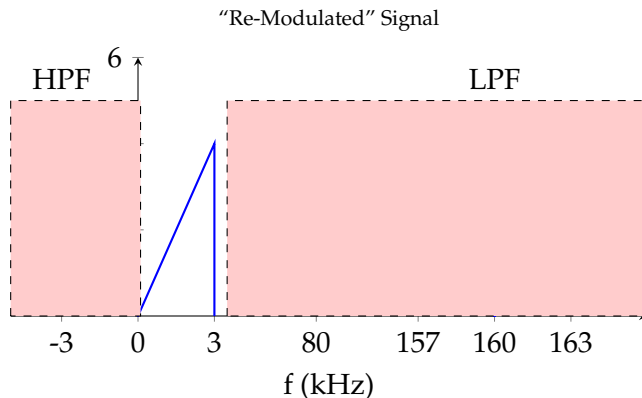Now we get rid of the stuff we don't want:



SYNCHRONOUS DETECTOR - FINAL FORM

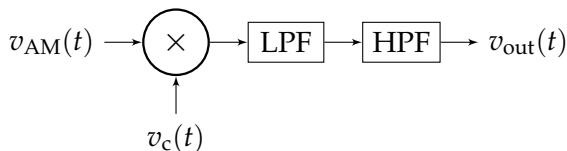
The final form of the synchronus detector is:



- LPF: $f_{cut} = \text{value slightly larger than } f_{m,max}$
- HPF: $f_{cut} = 10\text{Hz}$


SYNCHRONOUS EXAMPLE

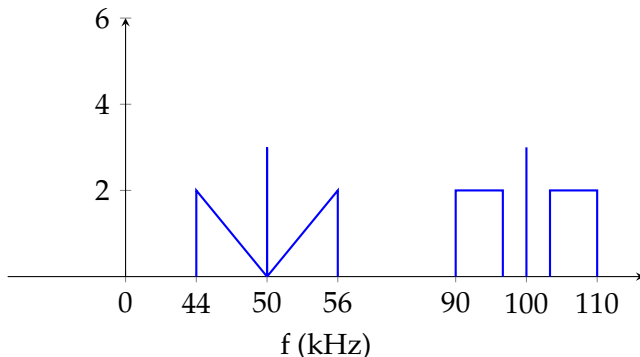Design a synchronous detector to recover the message signal centered at 50kHz.








SYNCHRONOUS EXAMPLE SOLUTION

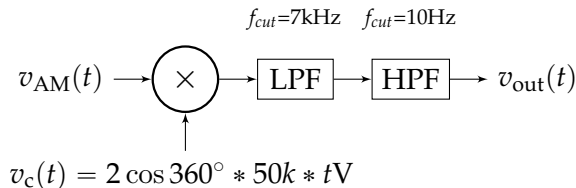The final form of the synchronus detector is:




DEMODULATING 100%/UNDERMODULATED SIGNALS

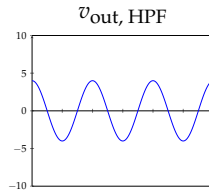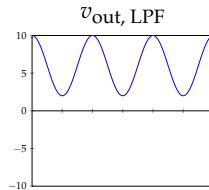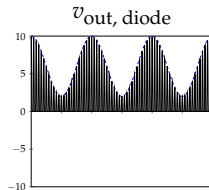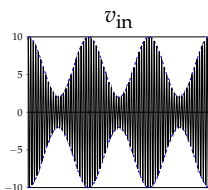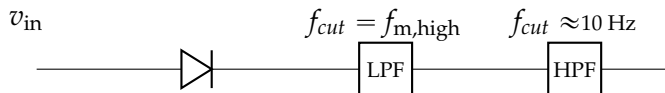

ENVELOPE DETECTION EXAMPLE

Determine the proper filter cutoff frequencies.



v_{in}

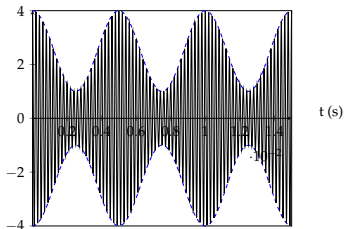


$$T_m = 5\text{ms} \implies f_m =$$

$$f_{\text{cut, LPF}} =$$

$$f_{\text{cut, HPF}} =$$

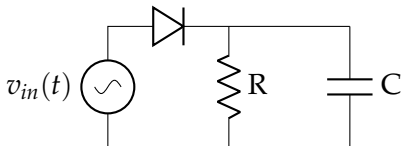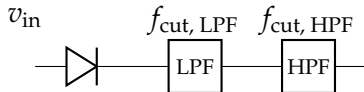


DEMODULATION EXAMPLE

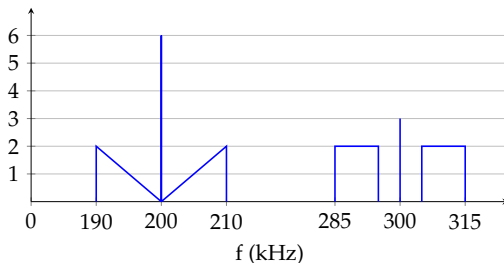

For $A_c = 2V$:

- What is the modulation index for each signal?
- What is the efficiency?
- Is the signal over-, under-, or fully-modulated?
- What demodulator(s) can you use for each signal?
- Design a demodulator for each signal


DEMODULATION EXAMPLE

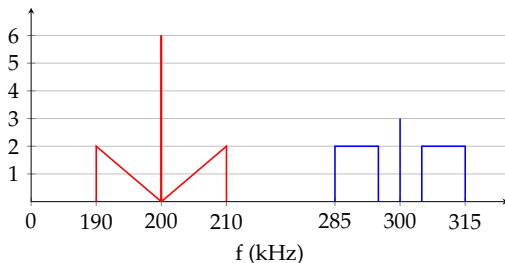

For $A_c = 2V$: (Signal centered at 200kHz)

- What is the modulation index for each signal? $\alpha_1 = \frac{2+2}{6} = 0.667$
- What is the efficiency? $\eta_1 = \frac{0.667^2}{0.667^2 + 2} = 18.2\%$
- Is the signal over-, **under**-, or fully-modulated?
- What demodulator(s) can you sue for each signal? **Synchronous or Envelope**
- Design a demodulator for each signal **Envelope, LPF @ ~ 11 kHz, HPF @ 10Hz**

DEMODULATION EXAMPLE

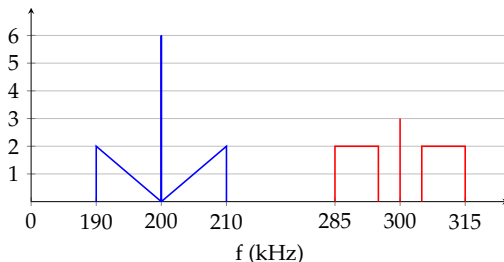

For $A_c = 2V$: (Signal centered at 300kHz)

- What is the modulation index for each signal? $\alpha = \frac{2+2}{3} = 1.333$
- What is the efficiency? $\eta_1 = \frac{1.333^2}{1.333^2 + 2} = 47\%$
- Is the signal **over**-, under-, or fully-modulated?
- What demodulator(s) can you sue for each signal? **Synchronous**
- Design a demodulator for each signal **Synchronous, multiplier @ 300kHz, LPF @ ~ 16 kHz, HPF @ 10Hz**

TRADEOFFS

Detector Type	Applicability	Receiver Complexity	Efficiency
<ul style="list-style-type: none">Envelope	<ul style="list-style-type: none">Fully modulatedUnder modulated	<ul style="list-style-type: none">CheapEasy to build	<ul style="list-style-type: none">Wasted power due to required bias
<ul style="list-style-type: none">Synchronous	<ul style="list-style-type: none">All types	<ul style="list-style-type: none">ExpensiveComplex to build	<ul style="list-style-type: none">Very efficient (up to 100%!)