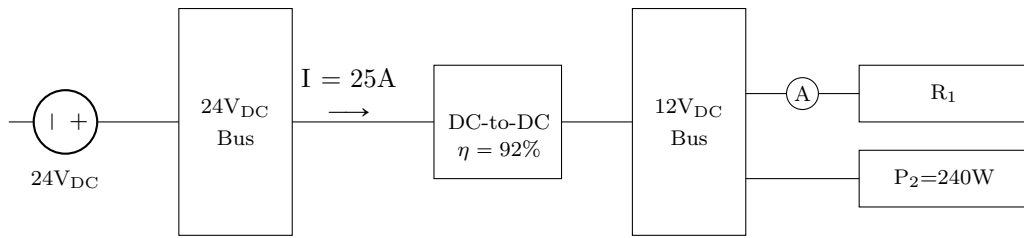


Name:

Documentation:

1. Analyze the following DC section of a power system.



- (a) Determine the power going into the DC/DC converter.

$$P_{\text{dc/dc, in}} =$$

- (b) Find the power out of the DC/DC converter.

$$P_{\text{dc/dc, out}} =$$


- (c) Determine the value of the unknown resistance R_1 (note that it consumes part of the power from Part (b)).

$$R_1 =$$

- (d) What would be a reasonable circuit breaker value to protect the R_1 load?

$$\text{Value} =$$

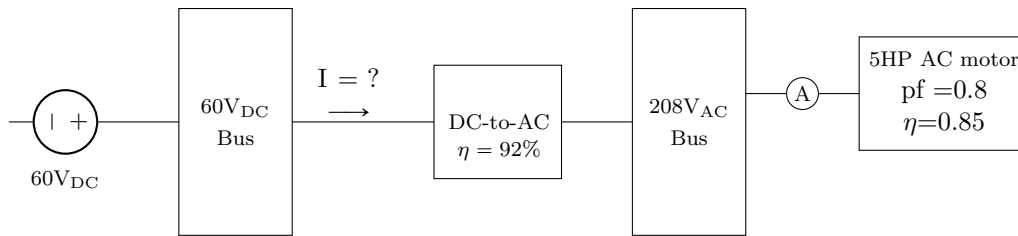2. Analyze the following section of a power system.



(a) Assuming the motor is operating at 5HP, find the real electrical power going into the motor.

$$P_{\text{motor, in}} =$$

(b) Find the real power going into the DC/AC inverter.

$$P_{\text{DC/AC}} =$$

(c) Determine the DC current into the DC/AC inverter and suggest a suitable circuit breaker value to protect it.


$$I_{\text{DC/AC, in}} =$$

$$\text{Fuse} =$$

(d) If we choose to allow $I = 90\text{A}$ (and the circuit breaker rating is adjusted appropriately), how much additional real power can be added to the 208V_{AC} bus at this value?

$$P =$$

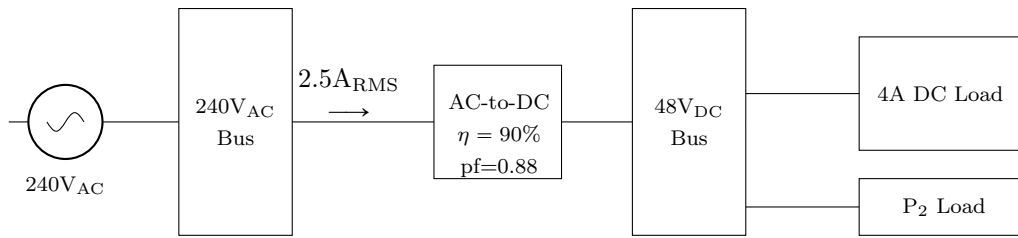3. Analyze the following section of a power system.



(a) Find the apparent power into the AC/DC converter.

$$S_{\text{AC/DC}} =$$

(b) Find the real power going into the AC/DC converter.

$$P_{\text{AC/DC, in}} =$$

(c) Find the real power out of the AC/DC converter.

$$P_{\text{AC/DC, out}} =$$

(d) Find the unknown power, P₂

$$P_2 =$$