

ECE 215 Spring 2025

Objective 1.6:
Transformers and
Power
Transmission




UNITED STATES
AIR FORCE
ACADEMY

Objective 1.6

I can use a transformer's turns ratio, input voltages and currents, and output voltages and currents to calculate the efficiency, source voltage, and current of a power transmission system with one or more transformers.

THE POWER GRID

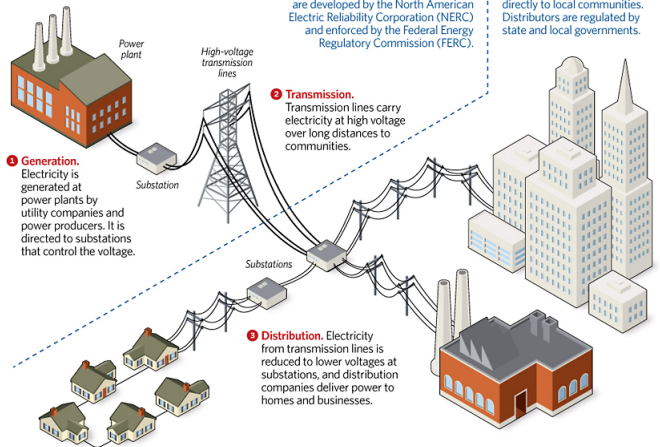
The Grid: How Electricity Is Distributed and Regulated



Note: FERC regulation does not include Texas.



BG 2959 heritage.org

DC POWER TRANSMISSION

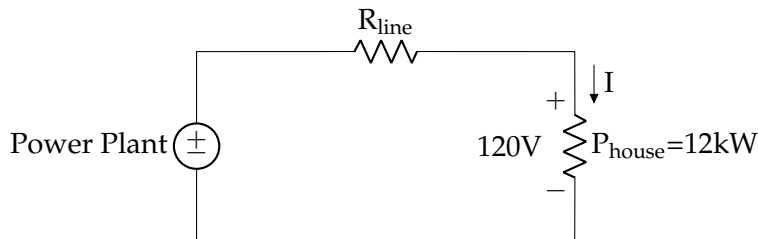


- Assume $R = 250\text{m}\Omega / \text{km}$, what is the efficiency for 20km distance?
- $I = \frac{P_{\text{house}}}{V_{\text{house}}} =$
- $P_{\text{line}} = I^2 R_{\text{line}} =$
- $\eta = \frac{P_{\text{useful}}}{P_{\text{total}}} = \frac{P_{\text{house}}}{P_{\text{total}}} =$

MAXWELL'S EQUATIONS

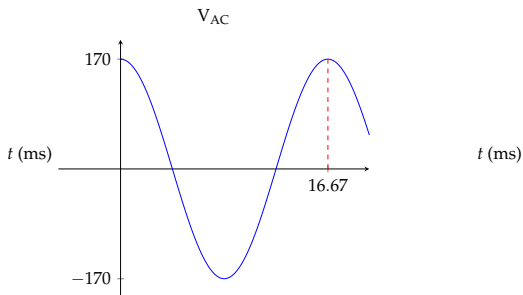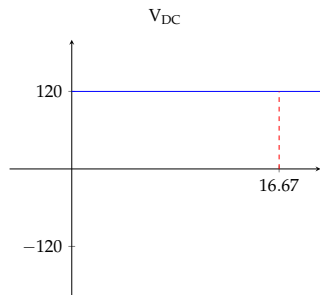


- Ampere says an electric current through a wire produces a **circulating** magnetic field ($\nabla \times \vec{H} \sim \vec{E}$)
- Farady says a **changing** magnetic field in a coil produces electric current ($\nabla \times \vec{E} \sim \frac{\partial \vec{H}}{\partial t}$)


MAXWELL APPLIED

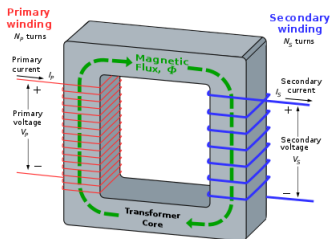

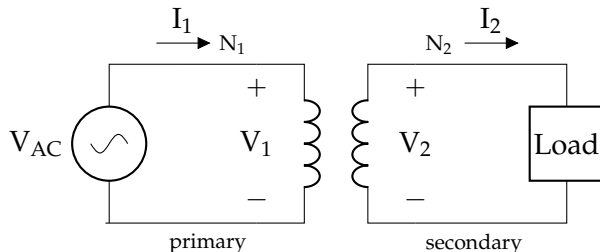- Changing magnetic flux (ϕ) produces voltage
- $V_{1,2} = N_{1,2} \frac{\partial \phi}{\partial t}$
- Flux on each side is equal




WHAT DOES A TRANSFORMER DO FOR US?

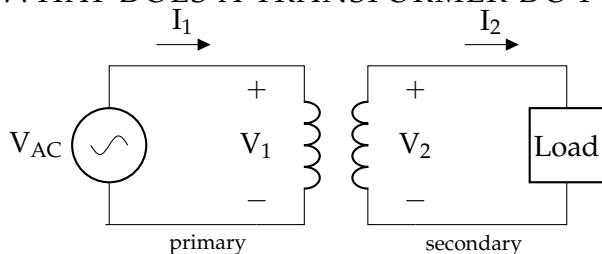


- Power on each side must be conserved
- $P_1 = P_2 \implies V_1 I_1 = V_2 I_2$
- Define the turns relationship as $a = \frac{N_1}{N_2} = \frac{V_1}{V_2}$
- $(a V_2) I_1 = V_2 I_2$
- $a = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$
- $a < 1$ is **step up** (why?)
- $a > 1$ is **step down** (why?)

FIND I_2 , a , P_{LINE} , AND η

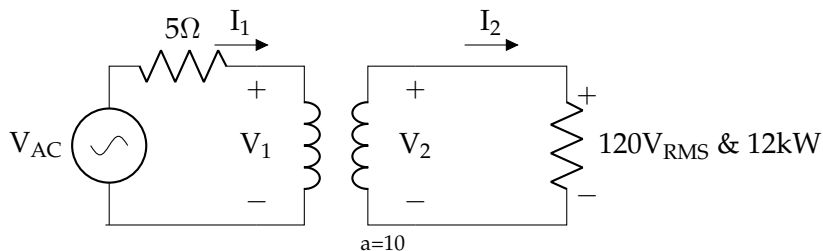


EXAMPLE 1

What is the efficiency of this circuit?

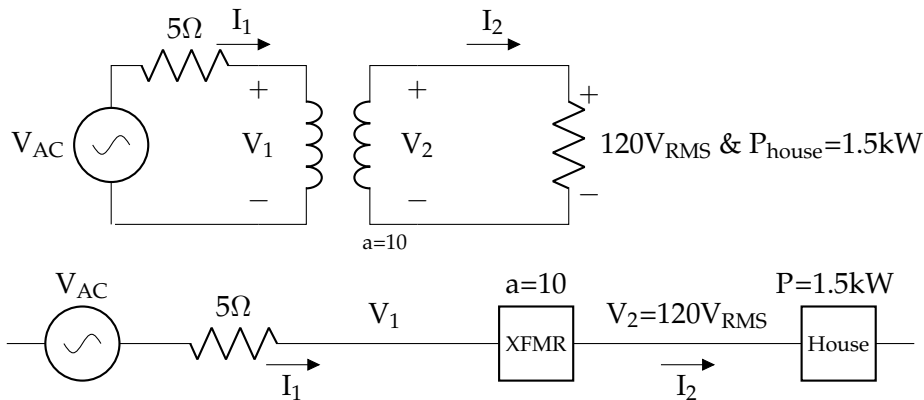


EXAMPLE 2

If we desired a transmission efficiency of 99%, what is the required turns ratio (a) and new source voltage?

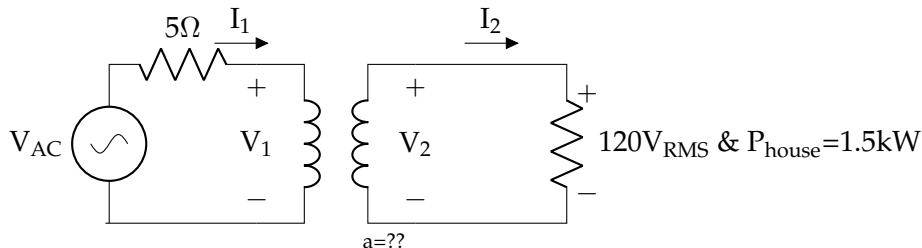


EXAMPLE 3

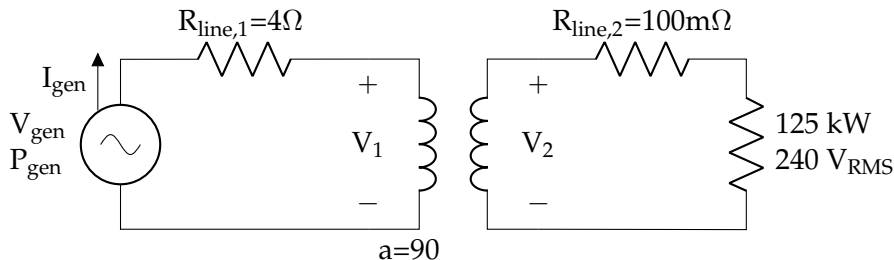

- What is the current provided by the generator?
- How much power is provided by the source?
- What is the voltage of the generator?
- What is the efficiency of the system?

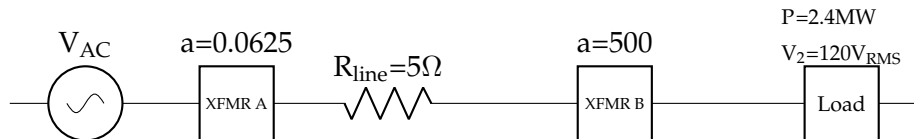EXAMPLE 4

Find the source voltage and system efficiency.



Steps:

- Find the load current
- Reflect XFMR B current and voltage
- Find R_{line} losses and voltage drop V_{line}
- Find voltage V_{A2} of secondary of XFMR A
- Reflect XFMR A current and voltage
- Find power produced at plant
- Find system efficiency