

Practice Problems

1. Calculate the cutoff frequency for a circuit with:

- a. $R = 1k\Omega$ and $C = 3nF$

$$f_{cutoff} = \frac{1}{2\pi RC} = \frac{1}{2\pi(1000)(3 \times 10^{-9})} = 53kHz$$

- b. $R = 5k\Omega$ and $C = 1.5\mu F$

$$f_{cutoff} = \frac{1}{2\pi RC} = \frac{1}{2\pi(5000)(1.5 \times 10^{-6})} = 21.22Hz$$

2. What should the resistor value be for the following filters:

- a. $f_{cutoff} = 1.5kHz$ and $C = 500 nF$

$$f_{cutoff} = \frac{1}{2\pi RC} - \text{this means } R = \frac{1}{2\pi f_{cutoff} C} = \frac{1}{2\pi(1500)(500 \times 10^{-9})} = 212\Omega$$

- b. $f_{cutoff} = 417Hz$ and $C = 56nF$


$$f_{cutoff} = \frac{1}{2\pi RC} - \text{this means } R = \frac{1}{2\pi f_{cutoff} C} = \frac{1}{2\pi(417)(56 \times 10^{-9})} = 6.8k\Omega$$

- c. $f_{cutoff} = 2kHz$ and $C = 500 \mu F$

$$f_{cutoff} = \frac{1}{2\pi RC} - \text{this means } R = \frac{1}{2\pi f_{cutoff} C} = \frac{1}{2\pi(2000)(500 \times 10^{-6})} = 159m\Omega$$

3. Are the circuits below high or low pass filters? How do you know?

(a)

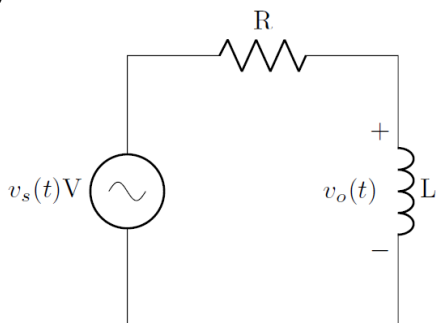


$$\frac{v_o(t)}{v_s(t)} = \frac{1}{1 + \frac{R}{j2\pi fL}}$$

when $f = 0$, $\frac{v_o(t)}{v_s(t)} = 0$ - When the frequency is low, the signal is not passed.

when $f = \infty$, $\frac{v_o(t)}{v_s(t)} = 1$ - When the frequency is high, the signal is passed.

High Pass Filter!

(b)

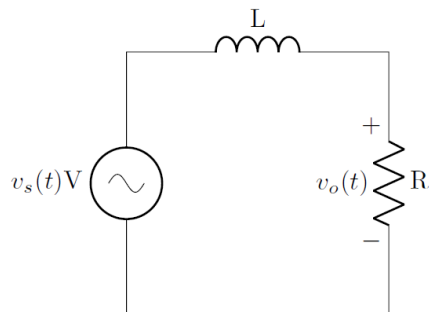


$$\frac{v_o(t)}{v_s(t)} = \frac{R}{j2\pi fL + R}$$

when $f = 0$, $\frac{v_o(t)}{v_s(t)} = 1$ - When the frequency is low, the signal is passed.

when $f = \infty$, $\frac{v_o(t)}{v_s(t)} = 0$ - When the frequency is high, the signal is not passed.

Low Pass Filter!

(c)

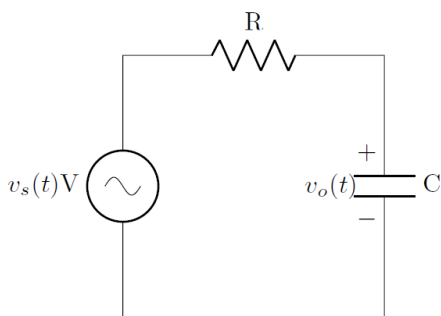


$$\frac{v_o(t)}{v_s(t)} = \frac{1}{j2\pi fCR + 1}$$

when $f = 0$, $\frac{v_o(t)}{v_s(t)} = 1$ - When the frequency is low, the signal is passed.

when $f = \infty$, $\frac{v_o(t)}{v_s(t)} = 0$ - When the frequency is high, the signal is not passed.

Low Pass Filter!

(d)

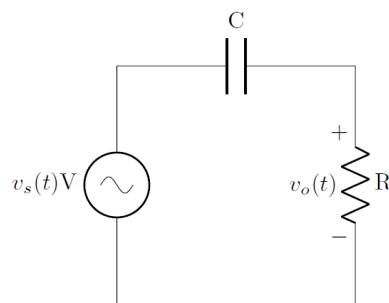

$$\frac{v_o(t)}{v_s(t)} = \frac{1}{1 + \frac{1}{j2\pi fRC}}$$

when $f = 0$, $\frac{v_o(t)}{v_s(t)} = 0$ - When the frequency is low, the signal is not passed.

when $f = \infty$, $\frac{v_o(t)}{v_s(t)} = 1$ - When the frequency is high, the signal is passed.

High Pass filter!

ECE 215

4. Calculate the cutoff frequency of the following systems.

(a) A transmission line modeled as an R-L circuit with $R=4\ \Omega$ and $L=5\mu\text{H}$.

$$f_{cutoff} = \frac{R}{2\pi L} = \frac{4}{2\pi(5 \times 10^{-6})} = 127\text{kHz}$$

(b) An R-C low pass filter with $R=60\ \Omega$ and $C=5\text{nF}$

$$f_{cutoff} = \frac{1}{2\pi RC} = \frac{1}{2\pi(60)(5 \times 10^{-9})} = 531\text{kHz}$$

(c) A C-R high pass filter with $R=100\ \Omega$ and $C=8\mu\text{F}$.

$$f_{cutoff} = \frac{1}{2\pi RC} = \frac{1}{2\pi(100)(8 \times 10^{-6})} = 199\text{Hz}$$

5. Your communications radio has a lower frequency bound of 800kHz. You know it has a capacitor value of 100nF, but what is the resistor value?


$$f_{cutoff} = \frac{1}{2\pi RC} - \text{this means } R = \frac{1}{2\pi f_{cutoff} C} = \frac{1}{2\pi(800000)(100 \times 10^{-9})} = 1.99\Omega$$

6. Design a high pass filter to get rid of a DC bias (0Hz) using a 100- Ω resistor you have available.

DC bias means $f = 0\text{Hz}$. This is impossible to attain, so let's choose our cutoff frequency to be 10Hz.
Let's just use a $R = 100\Omega$

$$f_{cutoff} = \frac{1}{2\pi RC} - \text{this means } C = \frac{1}{2\pi f_{cutoff} R} = \frac{1}{2\pi(10)(100)} = 159\mu\text{F}$$

7. For the circuit below, what is the magnitude of the gain, $\left| \frac{v_o}{v_{in}} \right|$, at 60 Hz?

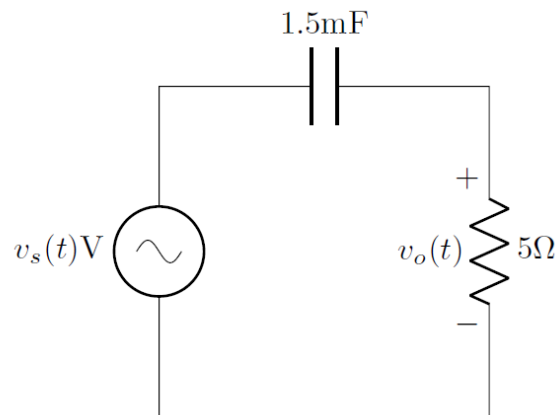

$$\frac{v_o(t)}{v_s(t)} = \frac{1}{1 + \frac{1}{j2\pi fRC}} = \frac{1}{1 + \frac{1}{j2\pi(60)(5) \cdot 0.0015F}} = 0.889 + j0.314 = 0.943 \angle 19.5^\circ$$

Because this problem asks for the magnitude, the answer is 0.942. This means the filter is passing 94.2% the signal, so 60 Hz is in the filter's pass band.