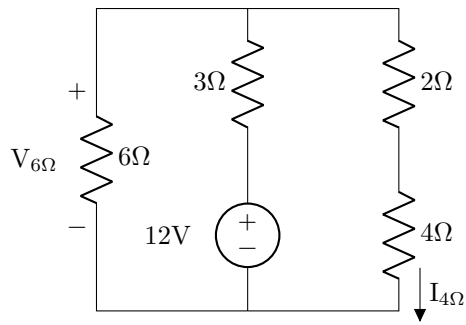


1. Analyze the following circuit:



(a) Find  $I_{4\Omega}$

$I_{4\Omega} =$

1 A

(b) Find  $V_{6\Omega}$

$V_{6\Omega} =$


6V

(c) Find the power delivered by the source.

$P_s =$

24W produced

2. Analyze the following circuit:

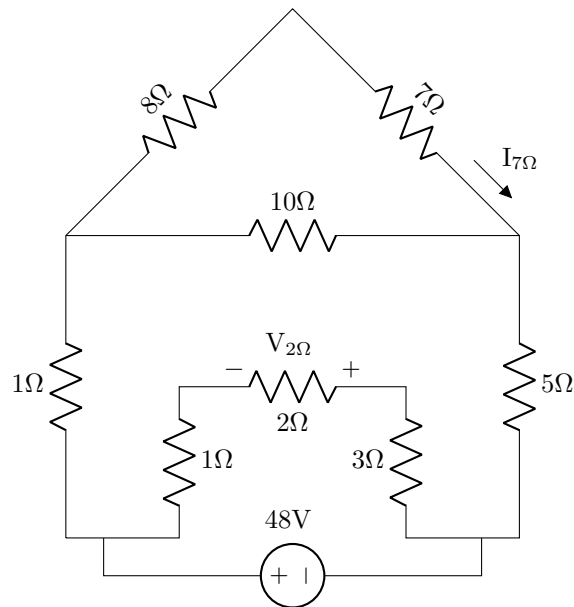

(a) Find  $V_{2\Omega}$  and  $I_{7\Omega}$ .

$$V_{2\Omega} =$$

16V

$$I_{7\Omega} =$$


1.6A

(b) What equivalent resistance does the 48V source “see”?

$$R_{eq} =$$

4Ω

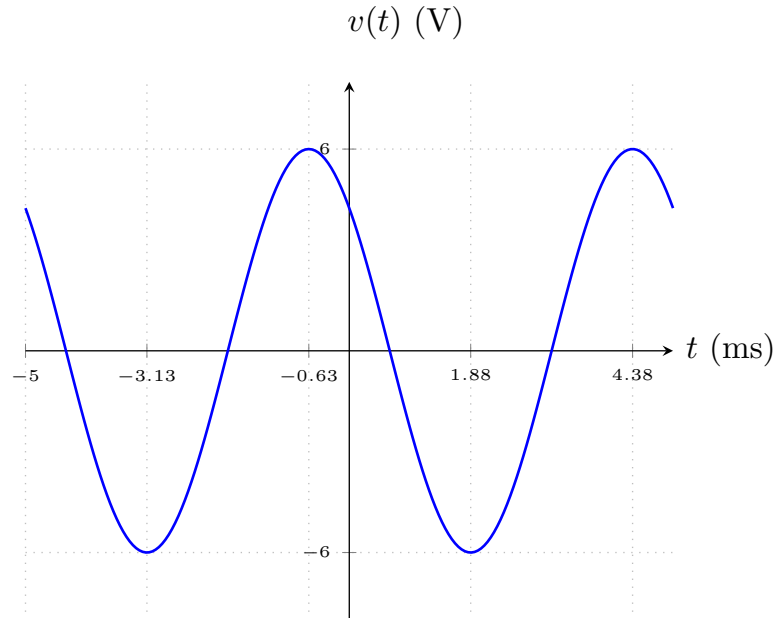3. Given the following sinusoidal waveform:



(a) Find its period and frequency in Hz (pay attention to the scaling).

T =

5 ms

f =

200 Hz

(b) What is its RMS value?

$V_{\text{RMS}} =$


4.243 V

(c) Write an expression for this signal in the form of  $V_{\text{pk}} \cos(\omega t + \phi_{\text{rad}})$

$V(t) =$

$6V \cos(\underbrace{1256.4}_{\text{rad/s}} t + \underbrace{.7854}_{\text{rad}})$

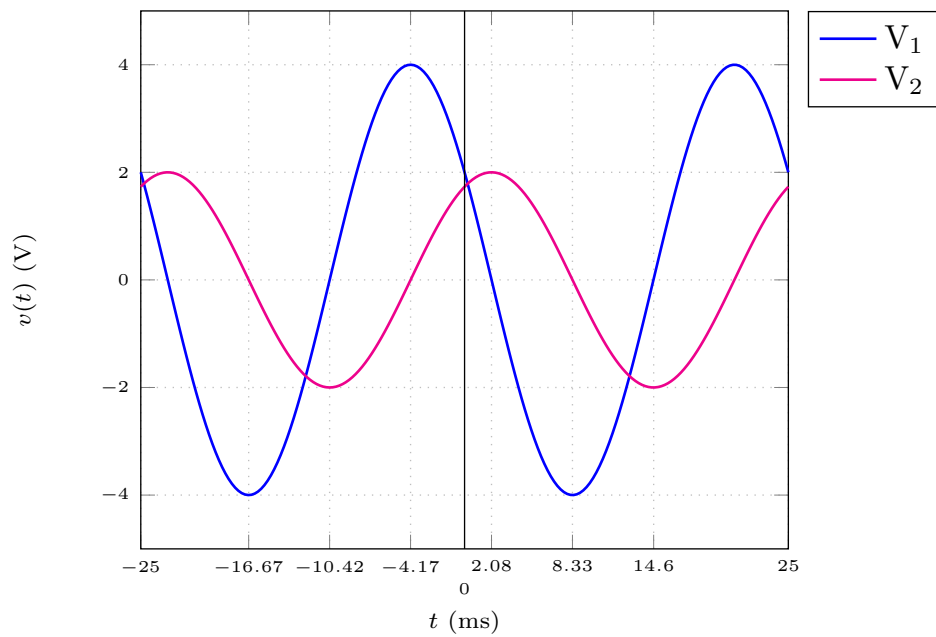4. Given the following two sinusoidal waveforms, which are at the same frequency:



(a) Find its period and frequency in Hz (pay attention to the scaling).

$T =$

25 ms

$f =$

40 Hz

(b) What is its RMS amplitude of each signal?

$V_1 =$

2.828 V

$V_2 =$


1.4142 V

(c) Which signal leads, and by how many **degrees**?

Answer =

$V_1$  leads  $V_2$   
90°

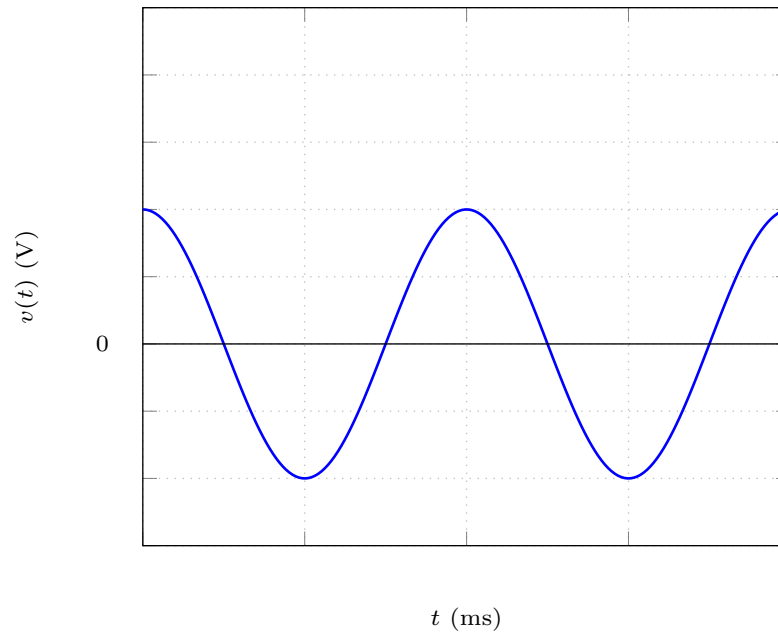5. Given the following oscilloscope waveform, where the vertical scale is set to 5V /div and the horizontal axis is set to 1ms/div:



- (a) Compute the frequency in Hz.

$f =$

500 Hz

- (b) Compute the RMS amplitude.

$V_{\text{RMS}} =$

7.071 V