

ECE 215 Spring 2025

Objective 1.3:

AC Circuit Analysis




UNITED STATES
**AIR FORCE
ACADEMY**

Objective 1.3


I can calculate the voltages, currents, instantaneous power, and average power associated with devices in a simple AC-powered circuit using tools such as KVL, KCL, voltage and current dividers, Ohm's Law, RMS values, and the power equation.

ANATOMY OF AC

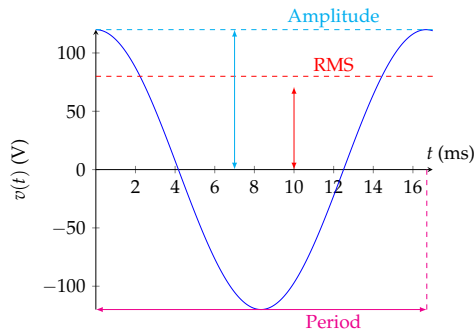

- $v(t) = V_{\text{bias}} + A \cos 2\pi f \cdot t + \Phi$
- $V_{\text{bias}} = \text{DC bias}$
- **Amplitude (A or V_{pk}) = peak strength of the signal**
- $2\pi = \text{converts period to } ^\circ (\text{sometimes } 360^\circ)$
- $f = \text{frequency} \left(\text{Hz} = \frac{1}{s} \right)$
- $t = \text{time}$
- **Period (T) = the time range over which the signal repeats $\left(T = \frac{1}{f} \right)$**
- $\Phi = \text{Phase shift} \left(\Phi = \frac{2\pi}{T} \Delta t \right)$
- **RMS Value (V_{rms}) = effective value of the signal**


AC EXAMPLE - SINE SIGNAL

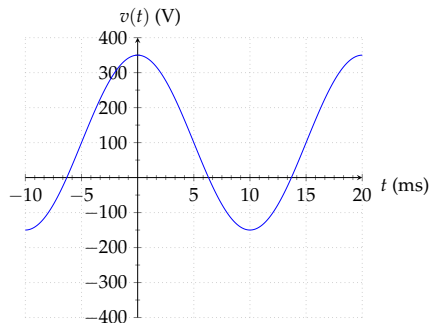

Questions:

- What is DC bias?
- What is the phase shift?
- What is the equation for this graph?
- What is the value of the signal at $t = 10\text{ms}$?
- What is the value of the signal at $t = 0\text{ms}$?


PHASE ANGLE

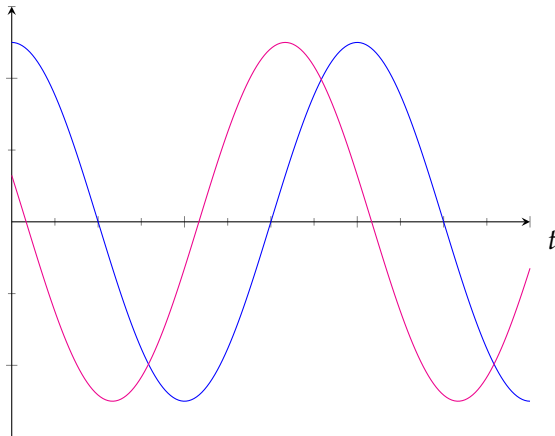 $v(t)$ (V)

Red leads Blue by 75 deg, or alternatively Blue lags Red by 75 deg.


AC AND OHM'S LAW - GOOD NEWS

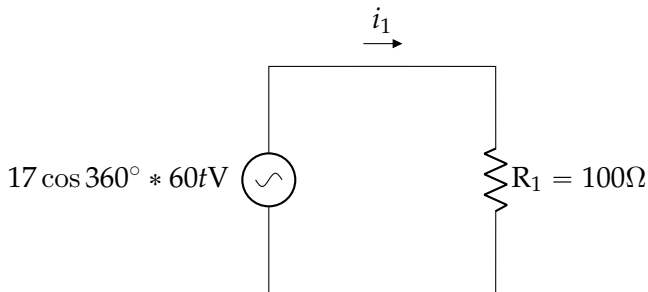- Ohm's Law still holds true!
- Must keep cosine term (still AC)
- Find i_1



AC AND OHM'S LAW - GOOD NEWS

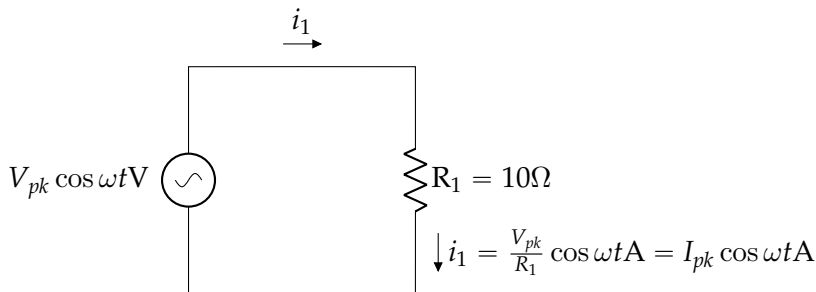- When looking at just a resistor, there is no phase difference between V_s and I_s
- No phase difference \rightarrow they are **in phase!**




- Recall $\omega = 2\pi f$

WHAT ABOUT POWER?

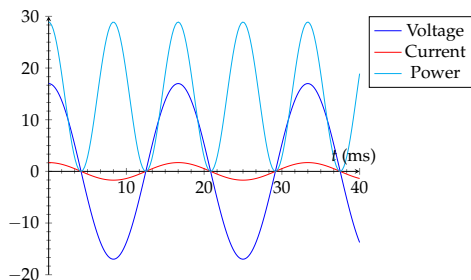Question: how much power is consumed by the resistor?

$$v(t) = 17 \cos 450t \text{ V} \quad i(t) = 1.7 \cos 450t \text{ A}$$



Average value of $P_{\text{inst}}(t)$?

Instantaneous Power

$$P_{\text{inst}}(t) = V_R I_R =$$

RMS

Definition

RMS value for a periodic waveform is the equivalent **DC** value that produces the same power effect.

$$\begin{aligned} V_{\text{RMS}} &= \sqrt{\frac{1}{T} \int_0^T [v(t)]^2 dt} = \sqrt{\frac{1}{T} \int_0^T [V_{\text{pk}} \cos \omega t + \theta]^2 dt} \\ &= \frac{V_{\text{pk}}}{\sqrt{2}} = 0.7071 V_{\text{pk}} \end{aligned}$$

REAL POWER

RMS

$$V_{\text{RMS}} = \sqrt{V_{\text{bias}}^2 + \frac{A^2}{2}} \quad \text{if } V_{\text{bias}} = 0, \text{ then:}$$
$$V_{\text{RMS}} = \frac{V_{\text{pk}}}{\sqrt{2}} = 0.707 * V_{\text{pk}}$$

Real Power

The average of the instantaneous power; represents the **real work** done by the electrical system.

$$P = \frac{1}{2} V_{\text{pk}} I_{\text{pk}} = \frac{1}{2} (\quad V_{\text{rms}}) (\quad I_{\text{rms}})$$