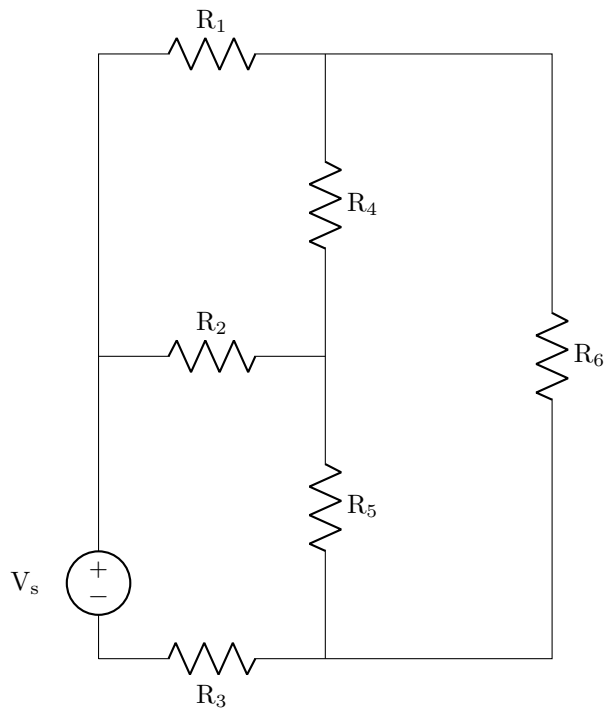


1. Given the circuit below:




(a) Identify the number of branches, the number of nodes, and the number of meshes.

Branches =  Nodes =  Meshes =

(b) Which resistors, if any, are in series with other resistors?

(A)  $R_1$  (B)  $R_2$  (C)  $R_3$  (D)  $R_4$  (E)  $R_5$  (F)  $R_6$

2. Given the following circuit:

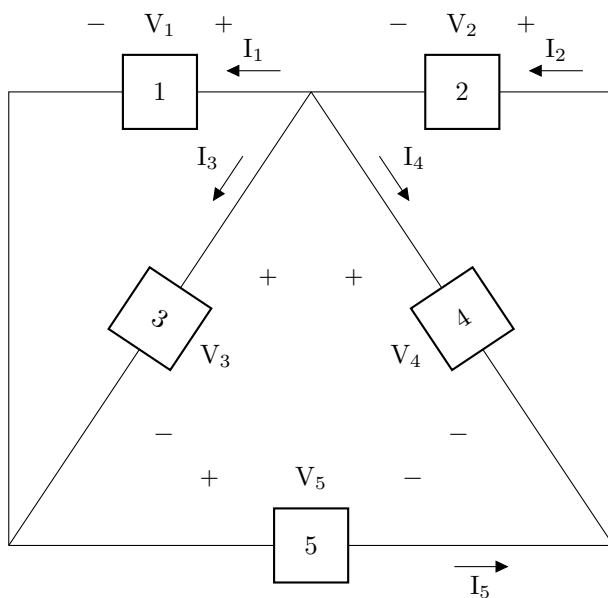

(a) How many nodes and meshes are there?

Nodes =  Meshes =

(b) If  $V_1 = 36\text{V}$  and  $V_2 = -18\text{V}$ , use KVL equations to solve for  $V_3$ ,  $V_4$ , and  $V_5$

$V_3 =$    $V_4 =$    $V_5 =$

(c) If  $I_1 = -15\text{A}$ ,  $I_2 = -3\text{A}$ , and  $I_5 = -9\text{A}$ , use KCL equations to solve for  $I_3$  and  $I_4$

$I_3 =$    $I_4 =$


- (d) Determine the power absorbed by each component (confirm that the sum of the powers absorbed must be zero).

$P_1 =$	<input type="text"/>	$P_2 =$	<input type="text"/>	$P_3 =$	<input type="text"/>
$P_4 =$	<input type="text"/>	$P_5 =$	<input type="text"/>		

- (e) Using the definition of parallel, which sets of components are in parallel?

Parallel =

3. Given the following circuit:

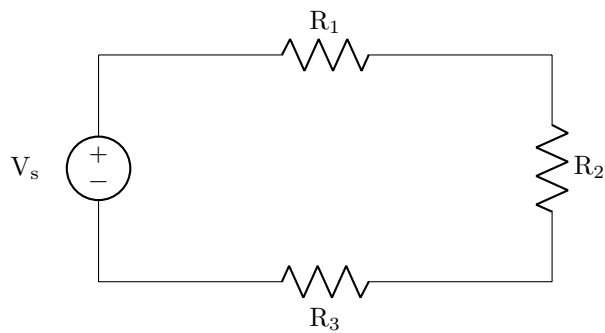

- (a) How many nodes and meshes are there?

Nodes =  Meshes =

- (b) Is the circuit series, parallel, or neither?

☐ (A) Series    ☐ (B) Parallel    ☐ (C) Neither


- (c) If  $V_s = 24\text{V}$  and  $R_1 = R_3 = 1\Omega$ , what value of  $R_2$  will make the current coming out of the voltage source equal 2A?

$R_2 =$

- (d) If  $V_s = 24\text{V}$  and  $R_1 = R_3 = 1\Omega$ , what new value of  $R_2$  will make the voltage across  $R_2$  equal 16V?

$R_2 =$

4. Given the following circuit:

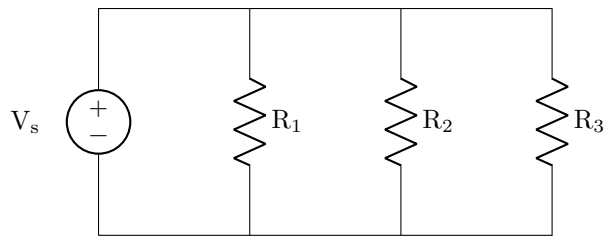

(a) How many nodes and meshes are there?

Nodes =  Meshes =

(b) Is the circuit series, parallel, or neither?

(A) Series    (B) Parallel    (C) Neither

(c) If  $V_s = 36\text{V}$ ,  $R_1 = 9\Omega$  and  $R_2 = 12\Omega$ , what value of  $R_3$  will make the current coming out of the voltage source equal to 13A?

$R_3 =$

- (d) Given  $R_1 = 9\Omega$ ,  $R_2 = 3\Omega$ , the current through  $R_1$  is 6A, and the source current is 33A, find the new value for  $V_s$ ,  $R_3$ , and the currents through  $R_2$  and  $R_3$ .  
(*Hint:*  $48V < V_s < 66V$ ,  $8A < I_3 < 11A$ )

$$V_s = \boxed{\phantom{000000}} \quad R_3 = \boxed{\phantom{000000}} \quad I_2 = \boxed{\phantom{000000}} \quad I_3 = \boxed{\phantom{000000}}$$